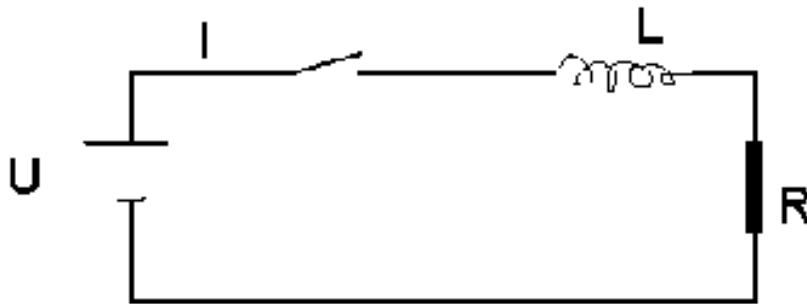


Current increase/ drop of a circuit with L and R



Summe aller Spannungen=0

$$U - I \cdot R - L \cdot \frac{dI}{dt} = 0$$

or
$$\frac{dI}{dt} + \frac{R}{L}(I - \frac{U}{R}) = 0 *$$

with $I - \frac{U}{R} = x \Rightarrow \frac{dx}{dt} = \frac{dI}{dt}$ or for
$$\frac{dx}{dt} + \frac{R}{L}x = 0$$

or: $\frac{dx}{x} = -\frac{R}{L}dt \Rightarrow \ln x = -\frac{R}{L}t + \ln A$ (constant of integration)

$\Rightarrow x = A \cdot e^{-\frac{R}{L}t} \Rightarrow I = \frac{U}{R} + A \cdot e^{-\frac{R}{L}t}$ for $t=0$ 'switch on', $I = 0$


$0 = \frac{U}{R} + A \Rightarrow A = -\frac{U}{R}$

thus $\Rightarrow I = \frac{U}{R}(1 - e^{-\frac{R}{L}t})$

for $t=0$ 'uncouple':


$t = 0, U = 0 \Rightarrow A = I_0$

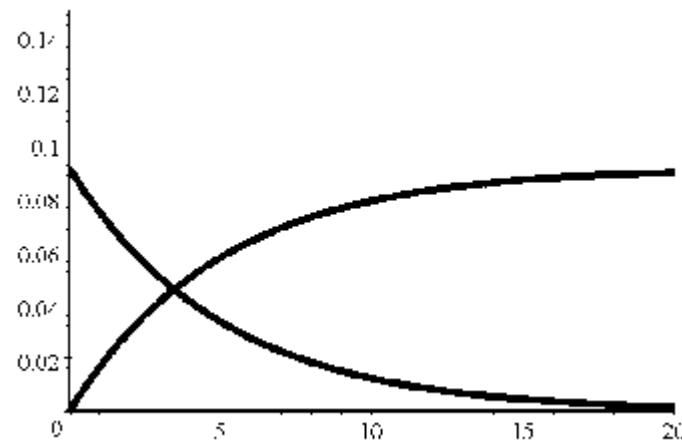and thus $I = I_0 \cdot e^{-\frac{R}{L}t}$



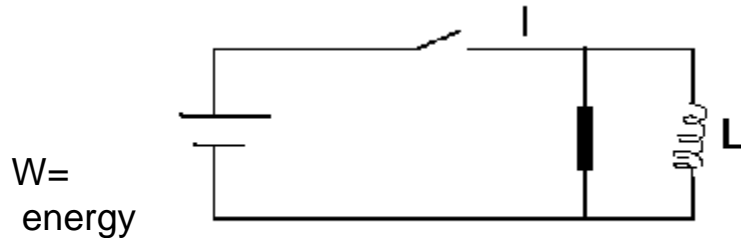8.10. Energy and density of energy in a magnetic field

Energy of breaking current: From magnetic field of coil



remember: Power $P = U \cdot I$

or with $U = R \cdot I$

$$P = I^2 \cdot R$$

$$W = \int_0^\infty I^2 \cdot R \cdot dt = \int I_0^2 \cdot e^{-2\frac{R}{L}t} \cdot R \cdot dt =$$

$$= R \cdot I_0^2 \cdot \int_0^\infty e^{-2\frac{R}{L}t} \cdot dt = R \cdot I_0^2 \left[-\frac{L}{2R} e^{-2\frac{R}{L}t} \right]_0^\infty = \frac{1}{2} L \cdot I_0^2$$

Magnetic field energy of a coil

For an elongate coil:

$$L = \mu_0 \frac{N^2 \cdot A}{l}$$

$$W = \frac{1}{2} \mu_0 \frac{N^2 \cdot A}{l} \cdot I^2 = \frac{1}{2} \underbrace{\mu_0 \frac{N \cdot I}{l}}_B \cdot \underbrace{\frac{N \cdot I}{l}}_{\frac{B}{\mu_0}} \cdot \underbrace{A \cdot l}_{\text{field volume}}$$

$$W = \frac{1}{2} \frac{B^2}{\mu_0} \cdot V \Rightarrow$$


energy density: $w_M = \frac{B^2}{2 \cdot \mu_0}$

compared to :
electric field

$$w_E = \frac{1}{2} \epsilon_0 E^2$$

9. Alternating voltage and alternating current

9.1.Exp:

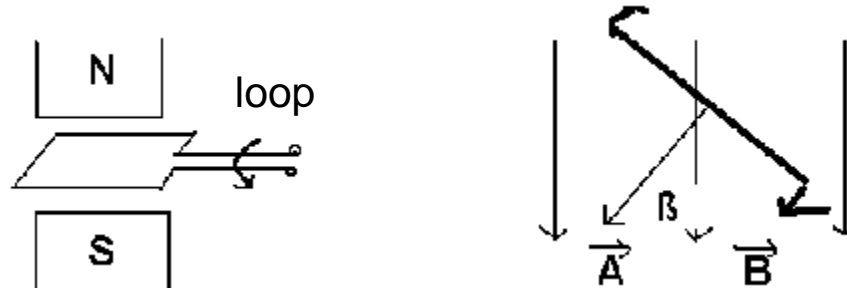


$$\Phi = \vec{B} \cdot \vec{A}; A : \text{area of coil}, B: \text{field} = \text{const.}$$

Turning the loop: $\Phi = B \cdot A \cdot \cos \beta$; be $\beta = \omega t$

$$\Phi(t) = B \cdot A \cdot \cos \omega t \Rightarrow U_{ind} = U_{\sim} = U(t) = -\frac{d\Phi}{dt} = \omega \cdot B \cdot A \cdot \sin \omega t$$

$$U(t) = N \cdot \omega \cdot B \cdot A \cdot \sin \omega t$$

flux/voltage

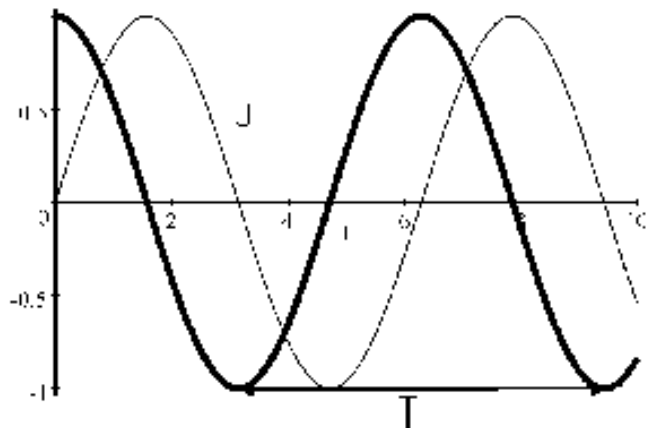

$$\nu = \frac{1}{T}, \omega = 2\pi\nu$$


9.2. Effektiv values of current and voltage

$$\underbrace{I_{\sim}} = \frac{U_{\sim}}{R} = \underbrace{\frac{U_0}{R}} \sin \omega t$$

Momentary value $= I_0(\text{ peak value})$

Ohmic resistance: voltage and current in phase

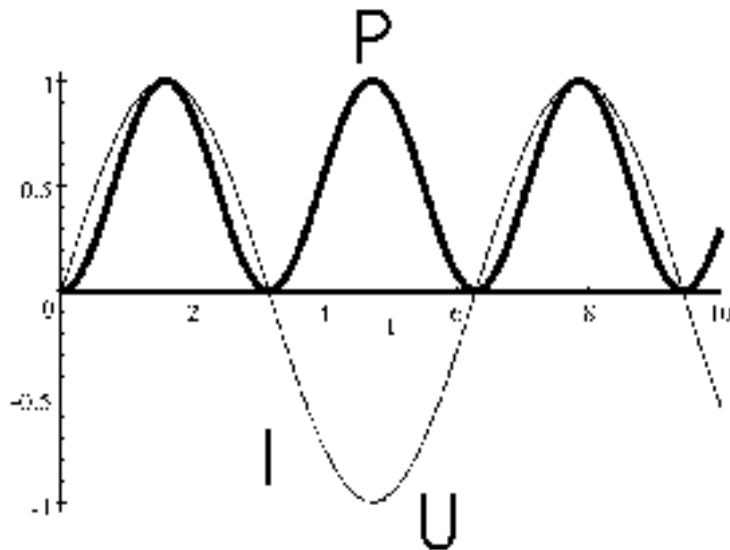Power consumption: $P = U \cdot I = U_0 \cdot \sin \omega t \cdot I_0 \cdot \sin \omega t = \frac{U_0^2}{R} \sin^2 \omega t$



Average: $\overline{P} = \frac{U_0^2}{R} \cdot \underbrace{\frac{1}{T} \int_0^T \sin^2 \omega t \cdot dt}$

0.5

$$= \frac{1}{2} \frac{U_0^2}{R} = \frac{1}{2} P_0$$

Def.: $\overline{P} = \frac{U_{eff}^2}{R}$ with


$$U_{eff} = \frac{1}{\sqrt{2}} U_0; I_{eff} = \frac{1}{\sqrt{2}} I_0$$

From socket:

$$U_{eff} = 220V \Rightarrow U_0 = 311V$$

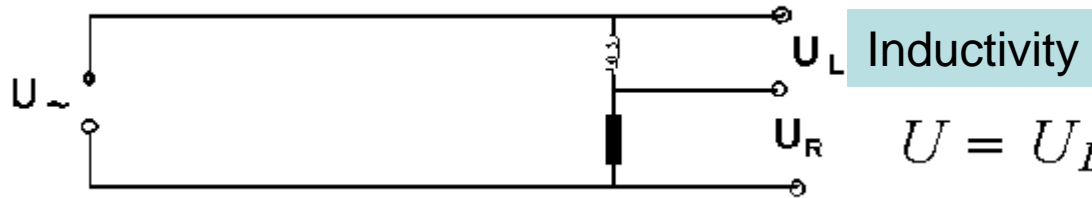9.3. Alternate current resistors

Exp: Phase shift between current and voltage



$$U = U_L + U_R = L \cdot \dot{I} + R \cdot I$$



Ansatz: $U = U_0 \cdot e^{i\omega t}$ $I = I_0 \cdot e^{i(\omega t - \varphi)}$ $\dot{I} = i\omega \cdot I_0 \cdot e^{i(\omega t - \varphi)} = i\omega \cdot I$

$$\Rightarrow U = \underbrace{(R + i\omega L)} \cdot I$$

Complex resistor Z

For current and volage:
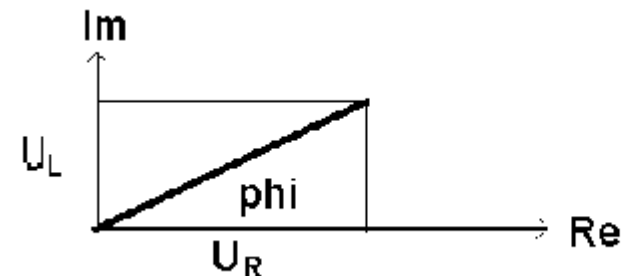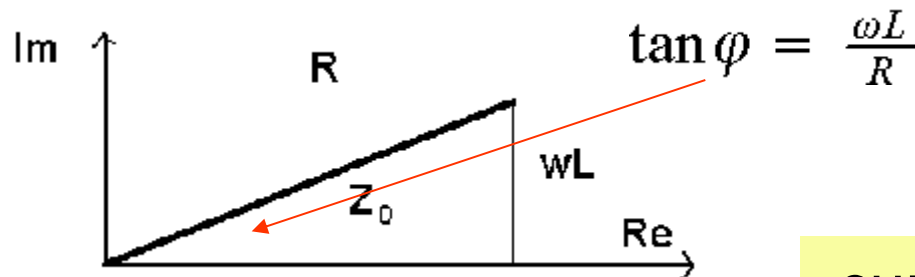
$$U = Z \cdot I; Z = \frac{U}{I} = \frac{U_0}{I_0} e^{i\varphi} = Z_0 e^{i\varphi}$$



$$U_L = i\omega L \cdot I \Rightarrow$$

current lags behind current : φ

Power: $P(t) = U \cdot I = U_0 \cdot \cos \omega t \cdot I_0 \cdot \cos(\omega t - \varphi)$

Average: $\bar{P} = \frac{1}{T} \int_0^T P(t) \cdot dt$ $\bar{P} = \frac{1}{2} P_0 \cdot \cos \varphi$


limiting cases: 1) $L=0 \Rightarrow \varphi = 0$ 2) $R=0 \Rightarrow \varphi = 90^\circ$

current lags behind voltage 90° nach

$$\bar{P} = 0$$

but idle power!

capacity:

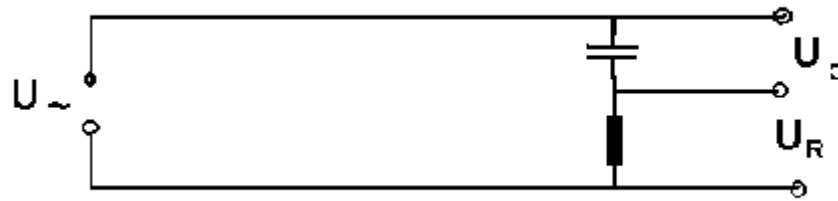

$$U = U_C + U_R, Q = C \cdot U_C \Rightarrow U_C = \frac{1}{C} \cdot Q = \frac{1}{C} \int I \cdot dt$$

$$\Rightarrow U = \frac{1}{C} \int I \cdot dt + R \cdot I$$

$$\dot{U} = \frac{1}{C} I + R \cdot \dot{I} \quad * \quad \text{Ansatz: } U = U_0 e^{i\omega t} \Rightarrow \dot{U} = i\omega U_0 e^{i\omega t} = i\omega U$$


$$I = I_0 e^{i(\omega t + \varphi)} \Rightarrow \dot{I} = i\omega I_0 e^{i(\omega t + \varphi)} = i\omega I \quad * \Rightarrow i\omega U = \frac{1}{C} I + R \cdot i\omega I$$

$$U = (R - i \frac{1}{\omega C}) I; Z = (R - i \frac{1}{\omega C}) : \text{ complex resistor}$$

$$Z = \frac{U}{I} = \frac{U_0}{I_0} e^{-i\varphi} = Z_0 e^{-i\varphi}$$

current is ahead of voltage!
again here

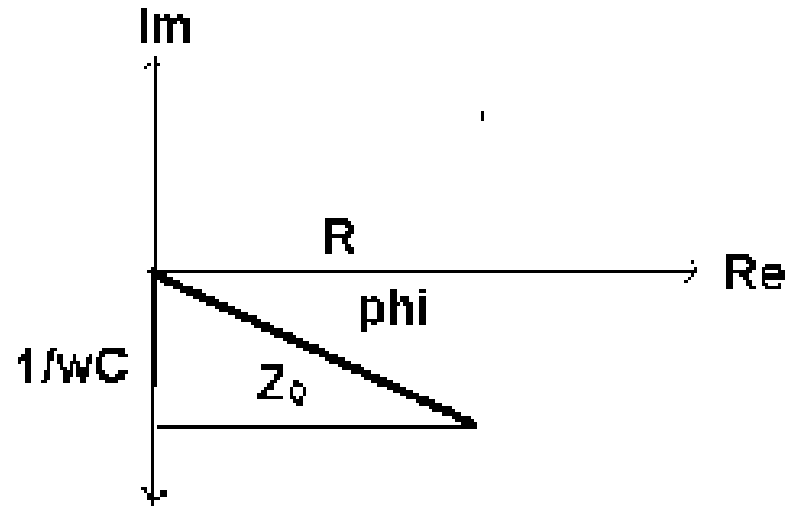
$$\overline{P} = \frac{1}{2} P_0 \cdot \cos \varphi$$



limiting case: $R=0$ current is ahead of voltage of 90° !

9.4. Electric oscillator circuit


a) undamped oscillator circuit

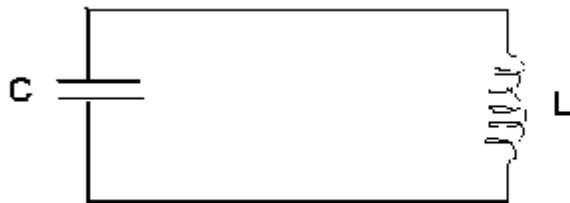

See also mechanics!

Energiesatz:
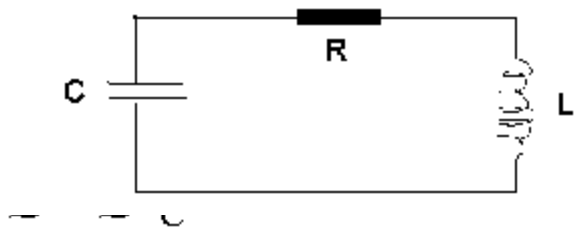
$$\underbrace{W_C}_{\frac{1}{2}CU^2} + \underbrace{W_L}_{\frac{1}{2}LI^2} = \text{const.}$$




Differentiate after t:

$$\frac{1}{C}Q + L \dot{I} = 0$$

$$\frac{1}{C} \dot{Q} + L \ddot{I} = 0 \Rightarrow \boxed{\ddot{I} + \frac{1}{LC}I = 0}$$

Solution: $I = I_0 e^{i\omega_0 t}$ with $\omega_0 = \frac{1}{\sqrt{LC}}$

b) Damped oscillations

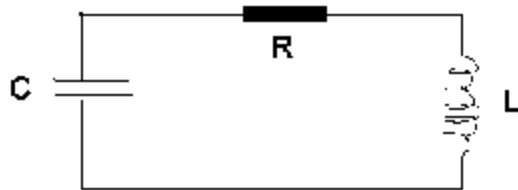

R: Energy pass to heat:

$$-\frac{d}{dt} \{W_C + W_L\} = I^2 R$$

$$-Q \cdot \dot{Q} \frac{1}{C} - L \cdot I \cdot \dot{I} = I^2 R$$

$$\frac{1}{C}Q + L \dot{I} + IR = 0$$

Differentiate: $\frac{1}{C} \dot{Q} + L \ddot{I} + R \dot{I} = 0$ or $L \ddot{I} + R \dot{I} + \frac{1}{C}I = 0$

Equation of oscillation for current!

Comparison with mechanics: $Q \simeq x; \vec{I} \simeq \vec{v};$

$$E_E = \frac{1}{2} \frac{Q^2}{C}; E_B = \frac{1}{2} L I^2 \quad m \ddot{x} + k \dot{x} + D x = 0 \Rightarrow L \simeq m, k \simeq R, \frac{1}{C} \simeq D$$

$$\text{Solution: } I = I_0 e^{-\delta t} e^{\pm i \omega t}; \delta = \frac{R}{2L}; \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$\omega = \omega_0 \sqrt{1 - \frac{CR^2}{4L}} \Rightarrow \text{3 cases: a) } R^2 < \frac{4L}{C} : \text{ case of oscillation}$$

$$\text{b) } R^2 = \frac{4L}{C} : \text{ Aperiodic critical damping} \quad I = I_0 \cdot e^{-\delta t}$$


$$\text{c) } R^2 > \frac{4L}{C} : \text{ critical damping: } \omega \text{ gets imaginary} \quad I = I_0 \cdot e^{-(\delta + \omega)t}$$

quality factor: $Q = \frac{\omega}{2\delta}$ s. Mechanics! lecture 16

c) Forced oscillations

$$U = U_0 \sin \omega t$$

power balance:

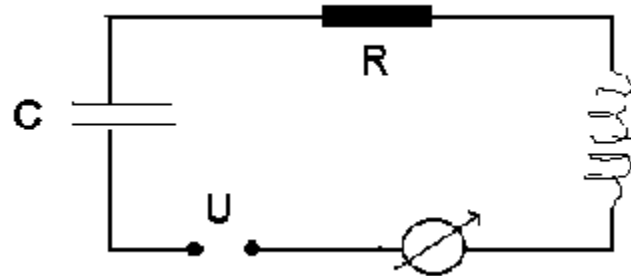

$$L \frac{d}{dt} \{W_C + W_L\} + I^2 R = U_0 \cdot I \cdot \sin \omega t$$

$$Q \cdot \dot{Q} \frac{1}{C} + L \cdot I \cdot \dot{I} + I^2 R = U_0 \cdot I \cdot \sin \omega t$$

$$Q \cdot \frac{1}{C} + L \cdot \dot{I} + I R = U_0 \cdot \sin \omega t : \quad \text{differentiate}$$

$$L \ddot{I} + R \dot{I} + \frac{1}{C} I = \omega \cdot U_0 \cdot \cos \omega t$$

$$\ddot{I} + \frac{R}{L} \dot{I} + \omega_0^2 \cdot I = \frac{1}{L} \omega \cdot U_0 \cdot \cos \omega t, *$$

solution wanted in the shape:

$$I = I_0 \sin(\omega t - \varphi) = I_0 \cdot [\sin \omega t \cos \varphi - \cos \omega t \sin \varphi]$$

$$\dot{I} = \omega \cdot I_0 \cos(\omega t - \varphi) = \omega \cdot I_0 [\cos \omega t \cos \varphi + \sin \omega t \sin \varphi]$$

$$\ddot{I} = -\omega^2 I_0 \sin(\omega t - \varphi) = -\omega^2 I_0 [\sin \omega t \cos \varphi - \cos \omega t \sin \varphi]$$

insert in $\quad \ast : I_0[-\omega^2 \sin \omega t \cos \varphi + \omega^2 \cos \omega t \sin \varphi] +$
 $\frac{R}{L} I_0[\omega \cos \omega t \cos \varphi + \omega \sin \omega t \sin \varphi] +$

$$\omega_0^2 I_0 \cdot [\sin \omega t \cos \varphi - \cos \omega t \sin \varphi] = \frac{1}{L} \omega \cdot U_0 \cdot \cos \omega t$$

true for "all" times \rightarrow coefficients of
 sin and cos on both sides of equation the same!

$$I_0[-\omega^2 \cos \varphi + \frac{R}{L} \omega \sin \varphi + \omega_0^2 \cos \varphi] = 0$$

$$I_0[\omega^2 \sin \varphi + \frac{R}{L} \omega \cos \varphi - \omega_0^2 \sin \varphi] = \frac{1}{L} \omega \cdot U_0 \quad \varphi$$



$$\tan \varphi = \frac{\omega^2 - \omega_0^2}{\frac{R\omega}{L}}; \sin \varphi = \frac{\omega^2 - \omega_0^2}{\sqrt{(\omega^2 - \omega_0^2)^2 + \frac{R^2 \omega^2}{L^2}}}; \cos \varphi = \frac{\frac{R\omega}{L}}{\sqrt{(\omega^2 - \omega_0^2)^2 + \frac{R^2 \omega^2}{L^2}}}$$

at resonance:

$$I_0 = \frac{\frac{1}{L} \omega \cdot U_0}{\sqrt{(\omega^2 - \omega_0^2)^2 + \frac{R^2 \omega^2}{L^2}}}$$

$$\omega = \omega_0 = \frac{1}{\sqrt{L \cdot C}}, \varphi = 0$$
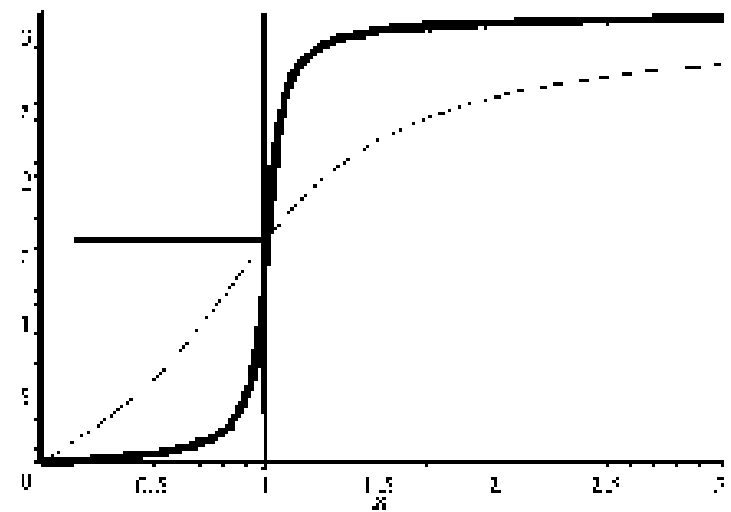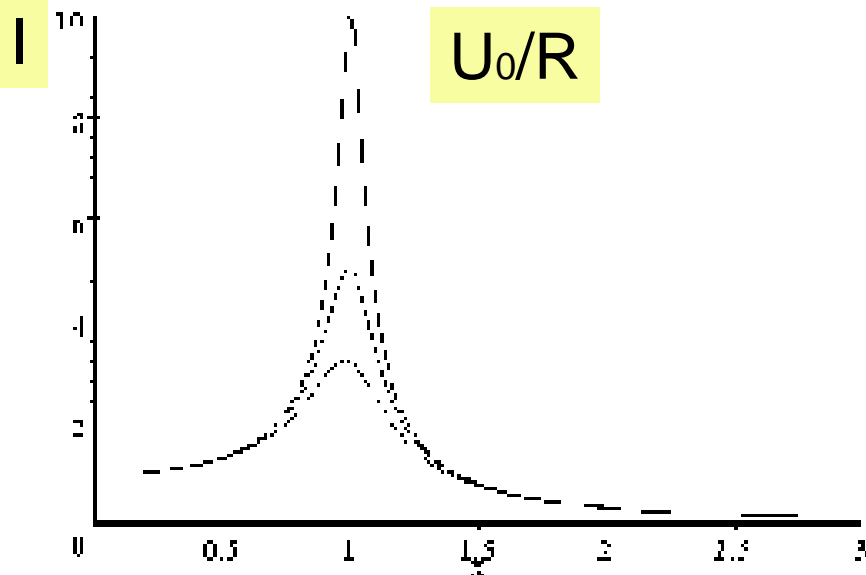
$$\Rightarrow I = \frac{U_0}{R} \cdot \cos \omega_0 t$$




voltage at R: $U_R = R \cdot I = U_0 \cdot \cos \omega_0 t$

.....at L: $U_L = L \cdot \dot{I} = -\omega_0 \cdot L \frac{U_0}{R} \sin \omega_0 t = -\frac{U_0}{R} \sqrt{\frac{L}{C}} \sin \omega_0 t$

.....at C: $U_C = \frac{1}{C} Q = \frac{1}{C} \int I \cdot dt = \frac{U_0}{R \cdot C} \int \cos \omega_0 t \cdot dt$
 $= \frac{1}{\omega_0 \cdot C} \frac{U_0}{R} \sin \omega_0 t = \frac{U_0}{R} \sqrt{\frac{L}{C}} \sin \omega_0 t$

in case of resonance $U_L = -U_C$

Parallelschwingkreis:

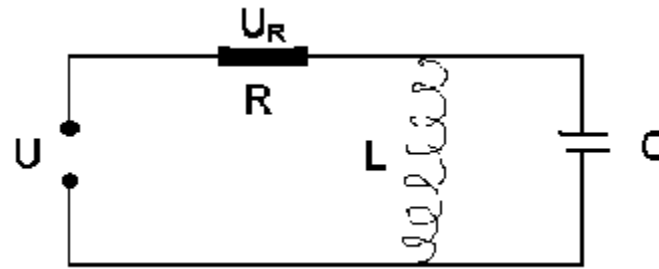

Gesamter Widerstand:


$$Z = R + Z_1 = Z_0 e^{i\varphi} \quad \frac{1}{Z_1} = \frac{1}{R_L} + \frac{1}{R_C} = \frac{1}{i\omega L} + i\omega C = i\left(\omega C - \frac{1}{\omega L}\right)$$

$$\Rightarrow Z_0 = \sqrt{R^2 + \frac{1}{\left(\frac{1}{\omega L} - \omega C\right)^2}} = R \sqrt{1 + \frac{\omega^2}{R^2 \left(\frac{1 - \omega^2 CL}{L}\right)^2}} =$$
$$R \sqrt{1 + \frac{\omega^2}{R^2 C^2 \left(\frac{1 - \omega^2 CL}{CL}\right)^2}} = R \sqrt{1 + \frac{\omega^2}{R^2 C^2 (\omega_0^2 - \omega^2)^2}}$$


$$\varphi = \arctan \left[\frac{\frac{1}{\frac{1}{\omega L} - \omega C}}{R} \right] = \varphi = \arctan \left[\frac{\frac{\omega L}{1 - \omega^2 CL}}{R} \right] =$$

$$\arctan \left[\frac{\frac{\omega L}{1 - \frac{\omega^2}{\omega_0^2}}}{R} \right] = \arctan \left[\frac{\omega L \omega_0^2}{R(\omega_0^2 - \omega^2)} \right] = \arctan \left[\frac{\omega}{RC(\omega_0^2 - \omega^2)} \right]$$

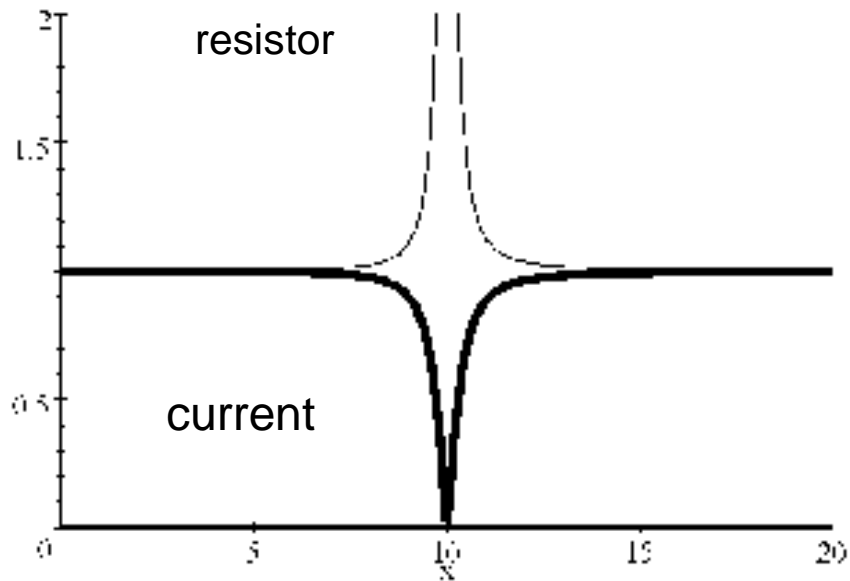Resonance: $\omega = \omega_0 \Rightarrow Z_0 \rightarrow \infty, I \rightarrow 0$



voltage:

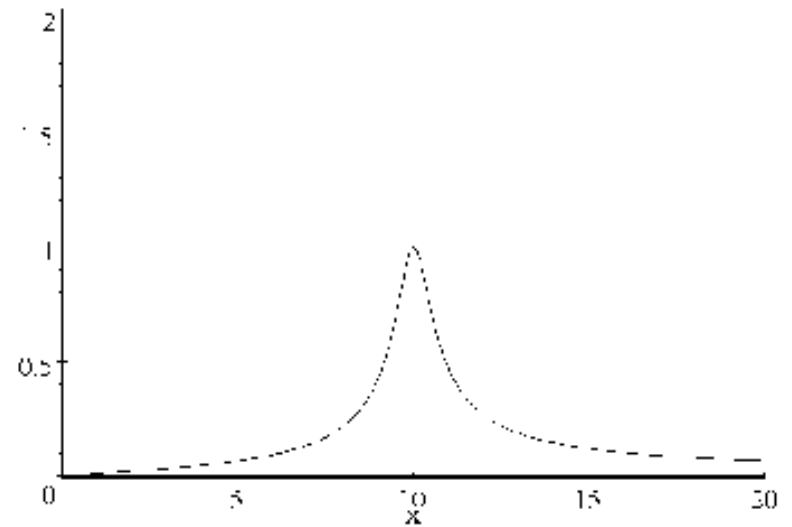

i.e.: Filter in TV, Radio etc.